

Integrated Circuit Design

Homework #1


Layout Reading

Deadline: Sep. 27


For the following layouts, please

- Draw the associated sticky diagram.
- Draw the circuit in transistor level.
- Describe the function of the circuits. (You can use Boolean equations or other descriptions)




1.

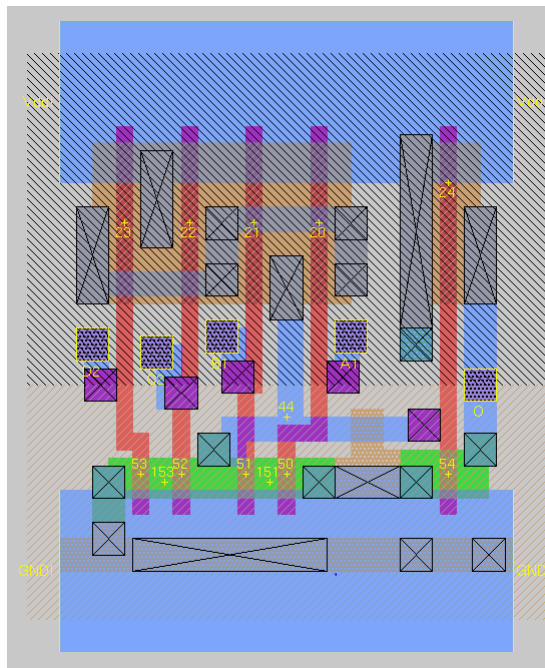

(c) $O = DC + AB$

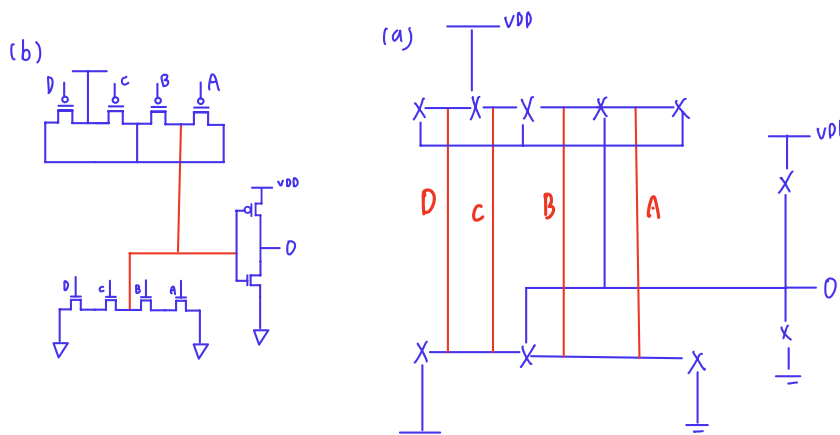

2.

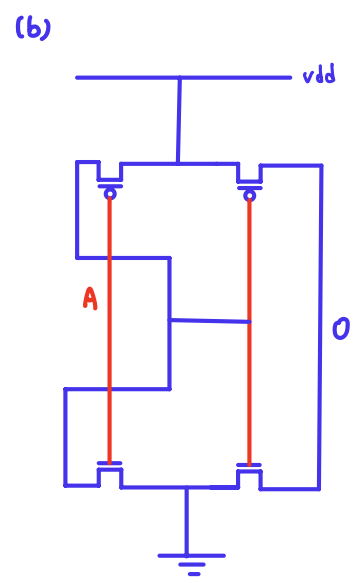
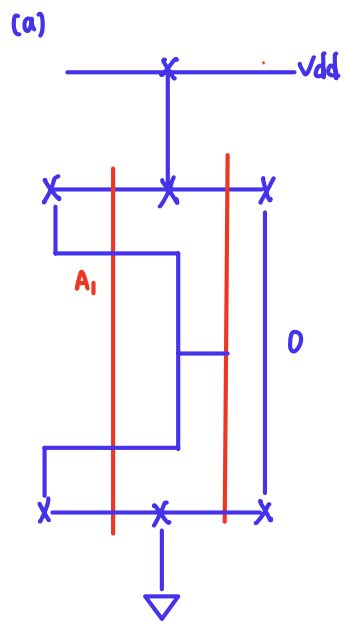
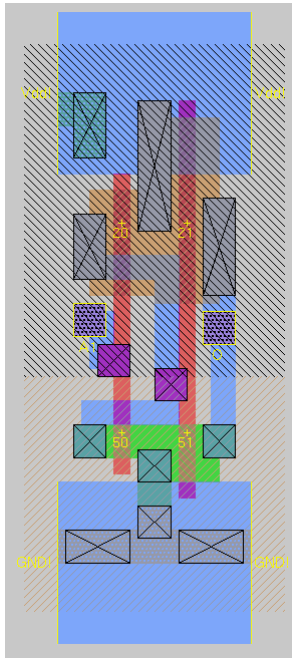


"A" is buffer

$$\therefore$$


A	0
0	0
1	1

3.

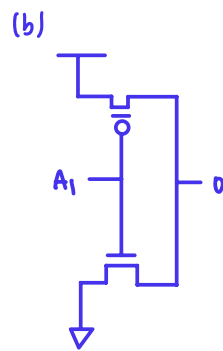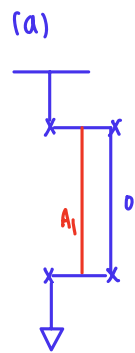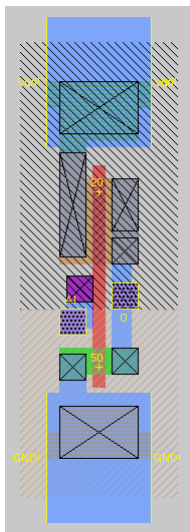


(c)
 $0 = \bar{A}_1$

4.

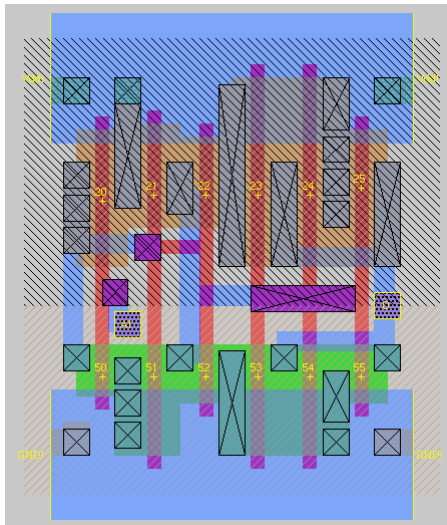


(a)

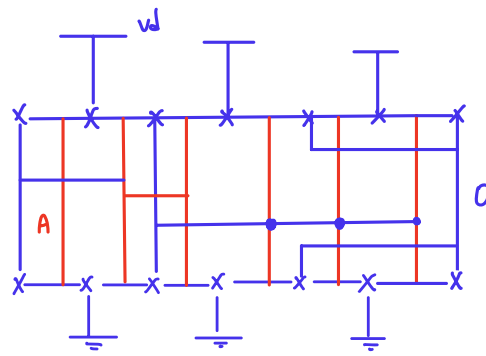


(c)

$$0 = \bar{A}$$


(b)

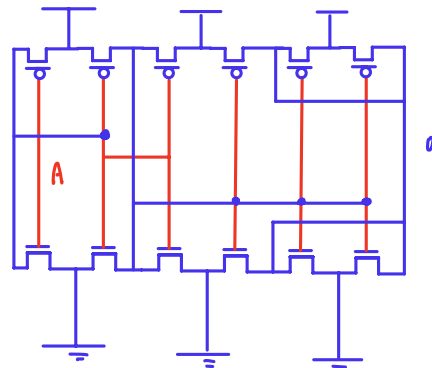


5.

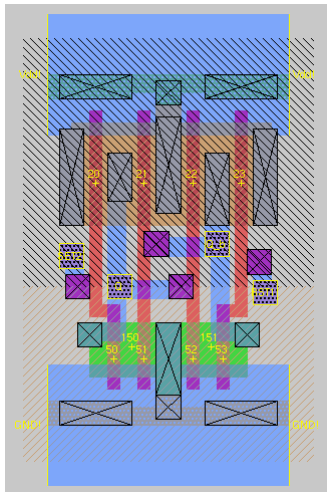

(a)

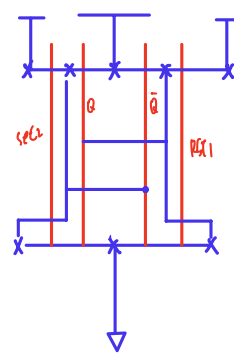


(b)

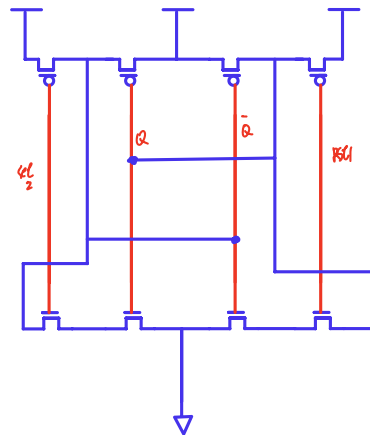


(c) SR latch


6.

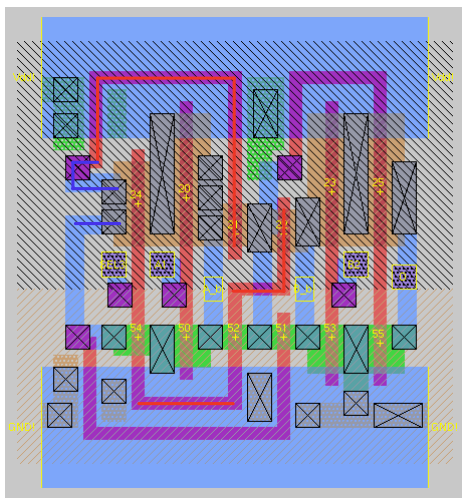

(a)

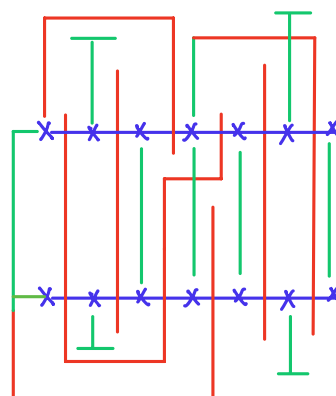


(b)

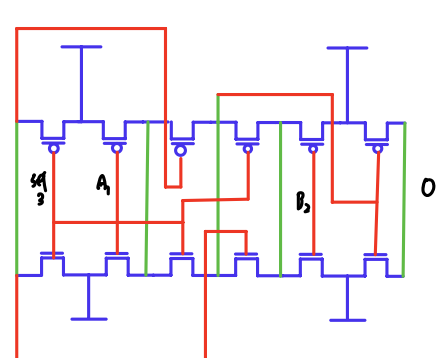


(c)

mux

7.

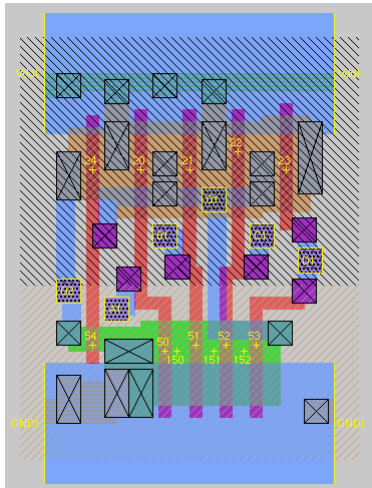


(a)

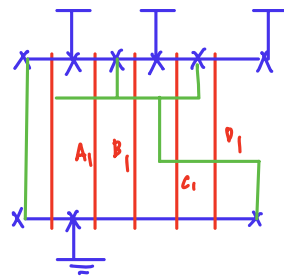


$$(c) O_1 = (ABCD)'$$

$$O_2 = ABCD$$


(b)

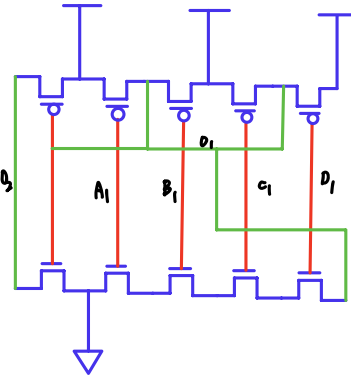


8.

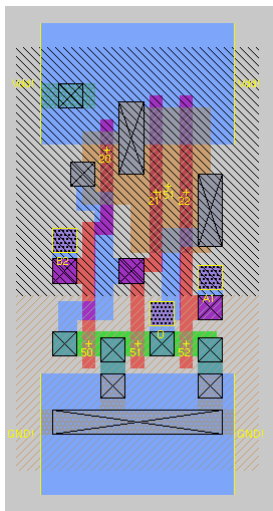

(a)

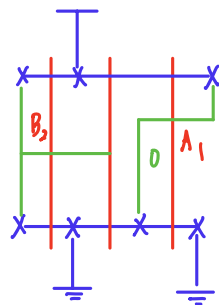


(b)

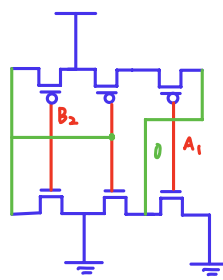


(c)

$$O = A'B$$

9.

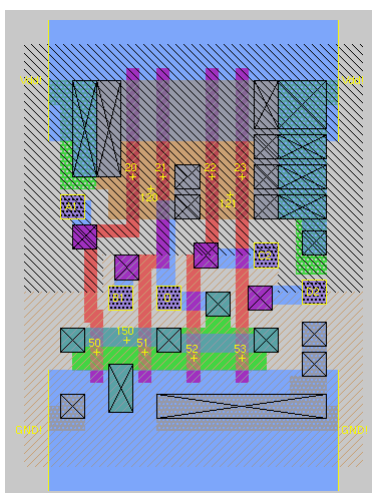


(a)

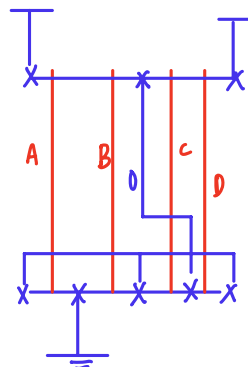



(c)

$$O = \overline{(A_1 + B_1) \cdot (C_2 + D_2)}$$


(b)

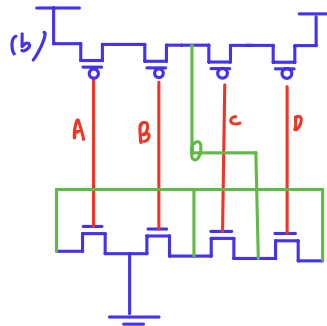

10.

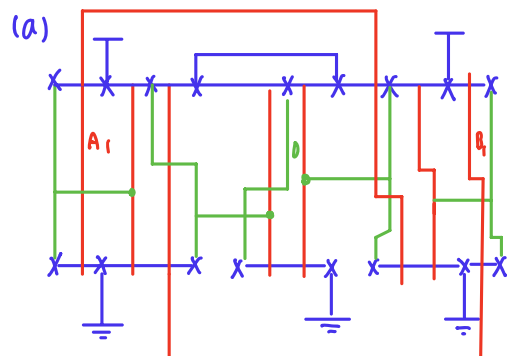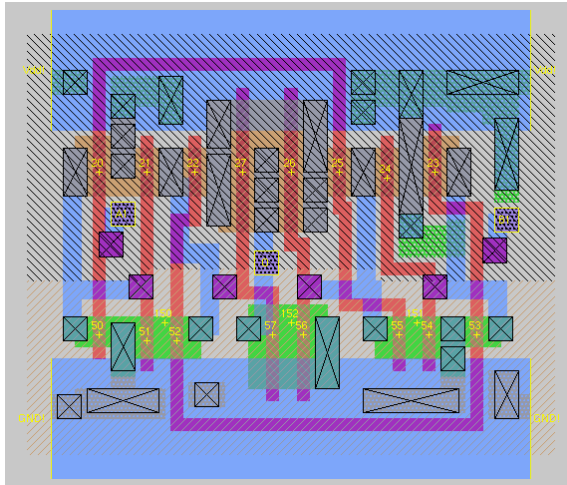

(b)

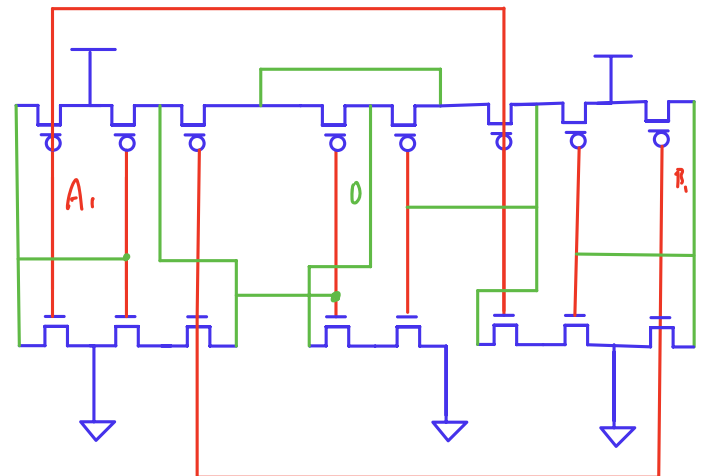

(c)

$$O = A_1' B_1 + A_1 B_1'$$